
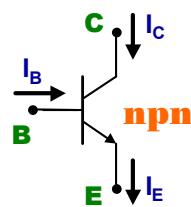


BJT

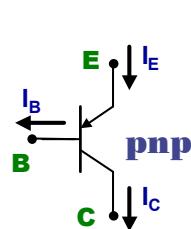


	Attiva	Saturazione	Spento
	$V_{BE} = 0.7 \text{ V}$	$V_{BE} = 0.7 \text{ V}$	$I_B = 0$
	$I_C = \beta_F I_B$	$V_{CE} = 0.2 \text{ V}$	$I_C = 0$
	$I_E = (\beta_F + 1)I_B$	$I_C < \beta_F I_B$	$I_E = 0$
	$V_{CE} > 0.2 \text{ V}$		$V_{BE} < 0.7 \text{ V}$



	Attiva	Saturazione	Spento
	$V_{BE} = -0.7 \text{ V}$	$V_{BE} = -0.7 \text{ V}$	$I_B = 0$
	$I_C = \beta_F I_B$	$V_{CE} = -0.2 \text{ V}$	$I_C = 0$
	$I_E = (\beta_F + 1)I_B$	$I_C < \beta_F I_B$	$I_E = 0$
	$V_{CE} < -0.2 \text{ V}$		$V_{BE} > -0.7 \text{ V}$



Piccolo segnale

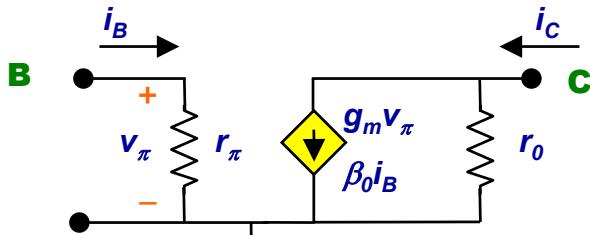

$$r_\pi = \frac{\beta_0}{g_m}$$

$$g_m = \frac{I_C}{V_T}$$

$$r_o = \frac{|V_A| + |V_{CE}|}{I_C}$$

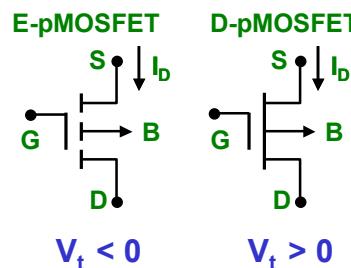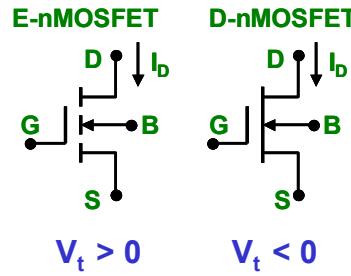

MOSFET

Lineare	Saturazione	Spento
$V_{GS} > V_t \text{ e}$ $V_{DS} < V_{GS} - V_t$ (o $V_{GD} > V_t$)	$V_{GS} > V_t \text{ e}$ $V_{DS} > V_{GS} - V_t$ (o $V_{GD} < V_t$)	$V_{GS} < V_t$ $I_D = 0$

$V_{GS} > 0, V_{DS} > 0, \lambda > 0$

Lineare	Saturazione	Spento
$V_{GS} < V_t \text{ e}$ $V_{DS} > V_{GS} - V_t$ (o $V_{GD} < V_t$)	$V_{GS} < V_t \text{ e}$ $V_{DS} < V_{GS} - V_t$ (o $V_{GD} > V_t$)	$V_{GS} > V_t$ $I_D = 0$


$V_{GS} < 0, V_{DS} < 0, \lambda < 0$

$$I_{DSS} = \frac{1}{2} k'_{n,p} \left(\frac{W}{L} \right) V_t^2$$

$$k'_{n,p} = \mu_{n,p} C_{OX}$$

$$\text{Saturazione}$$
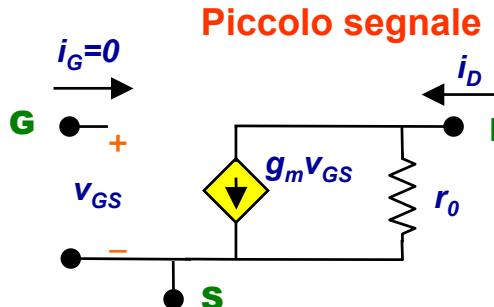
$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_t} \right)^2 (1 + \lambda V_{DS})$$




$$\text{Piccolo segnale}$$


$$g_m = \frac{2}{|V_t|} \sqrt{I_{DSS} I_D (1 + \lambda V_{DS})}$$

$$r_o = \frac{1}{|\lambda| + |V_{DS}|} \approx \frac{1}{|\lambda| I_D}$$


E-nMOSFET

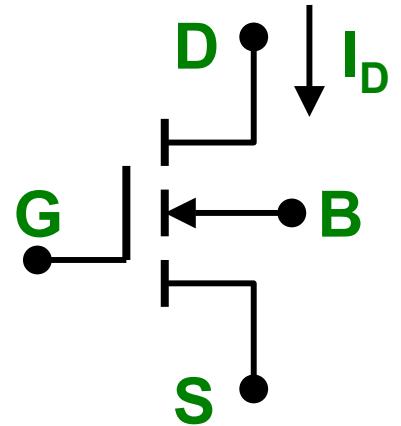


D-nMOSFET

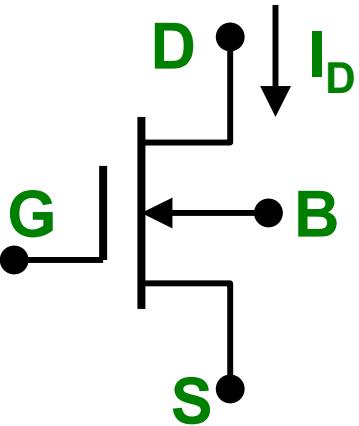


n - JFET

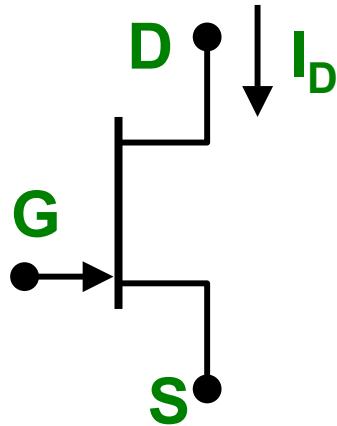

E-pMOSFET

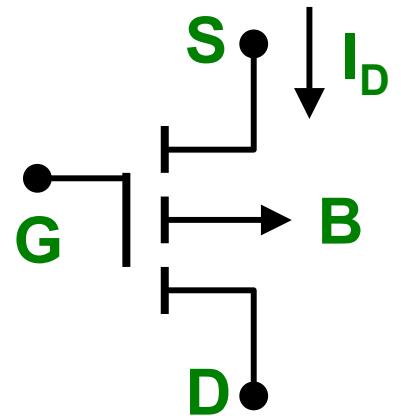

D-pMOSFET

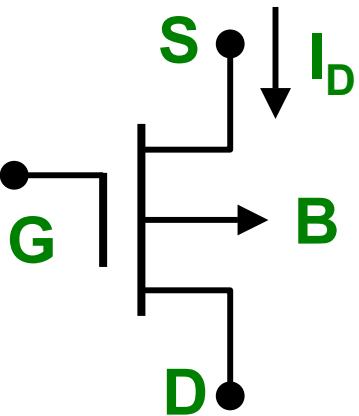

p - JFET

