

Circuit Element Variations

- All electronic components have manufacturing tolerances.
 - Resistors can be purchased with $\pm 10\%$, $\pm 5\%$, and $\pm 1\%$ tolerance. (IC resistors are often $\pm 10\%$.)
 - Capacitors can have asymmetrical tolerances such as $+20\%/-50\%$.
 - Power supply voltages typically vary from 1% to 10%.
- Device parameters will also vary with temperature and age.
- Circuits must be designed to accommodate these variations.
- We will use worst-case and Monte Carlo (statistical) analysis to examine the effects of component parameter variations.

Tolerance Modeling

- For symmetrical parameter variations
$$P_{\text{NOM}}(1 - \epsilon) \leq P \leq P_{\text{NOM}}(1 + \epsilon)$$
- For example, a 10K resistor with $\pm 5\%$ percent tolerance could take on the following range of values:

$$10\text{k}(1 - 0.05) \leq R \leq 10\text{k}(1 + 0.05)$$

$$9,500 \Omega \leq R \leq 10,500 \Omega$$

Circuit Analysis with Tolerances

- Worst-case analysis
 - Parameters are manipulated to produce the worst-case min and max values of desired quantities.
 - This can lead to overdesign since the worst-case combination of parameters is rare.
 - It may be less expensive to discard a rare failure than to design for 100% yield.
- Monte-Carlo analysis
 - Parameters are randomly varied to generate a set of statistics for desired outputs.
 - The design can be optimized so that failures due to parameter variation are less frequent than failures due to other mechanisms.
 - In this way, the design difficulty is better managed than a worst-case approach.




Worst Case Analysis Example

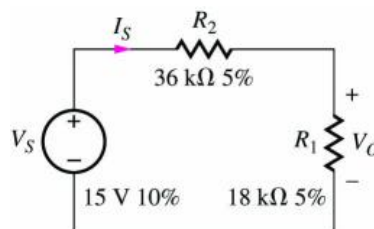Problem: Find the nominal and worst-case values for output voltage and source current.

Solution:

- **Known Information and Given Data:** Circuit topology and values in figure.
- **Unknowns:** V_o^{nom} , V_o^{min} , V_o^{max} , I_S^{nom} , I_S^{min} , I_S^{max} .
- **Approach:** Find nominal values and then select R1, R2, and Vs values to generate extreme cases of the unknowns.
- **Assumptions:** None.
- **Analysis:** Next slides...



Nominal voltage solution:


$$\begin{aligned}
 V_o^{nom} &= V_S^{nom} \frac{R_1^{nom}}{R_1^{nom} + R_2^{nom}} \\
 &= 15V \frac{18k\Omega}{18k\Omega + 36k\Omega} = 5V
 \end{aligned}$$



Worst-Case Analysis Example (cont.)

Nominal Source current:
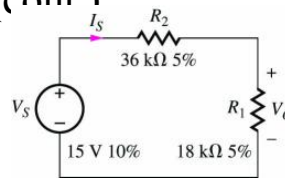
$$I_S^{nom} = \frac{V_S^{nom}}{R_1^{nom} + R_2^{nom}} = \frac{15V}{18k\Omega + 36k\Omega} = 278\mu A$$



Rewrite V_o to help us determine how to find the worst-case values.

$$V_o = V_S \frac{R_1}{R_1 + R_2} = \frac{V_S}{1 + \frac{R_2}{R_1}}$$

V_o is maximized for max V_S , R_1 and min R_2 .
 V_o is minimized for min V_S , R_1 , and max R_2 .

$$V_o^{\max} = \frac{15V(1.1)}{1 + \frac{36K(0.95)}{18K(1.05)}} = 5.87V$$

$$V_o^{\min} = \frac{15V(0.95)}{1 + \frac{36K(1.05)}{18K(0.95)}} = 4.20V$$

Worst-Case Analysis Example (cont.)

Worst-case source currents:

$$I_S^{\max} = \frac{V_S^{\max}}{R_1^{\min} + R_2^{\min}} = \frac{15V(1.1)}{18k\Omega(0.95) + 36k\Omega(0.95)} = 322\mu A$$

$$I_S^{\min} = \frac{V_S^{\min}}{R_1^{\max} + R_2^{\max}} = \frac{15V(0.9)}{18k\Omega(1.05) + 36k\Omega(1.05)} = 238\mu A$$


Check of Results: The worst-case values range from 14-17 percent above and below the nominal values. The sum of the three element tolerances is 20 percent, so our calculated values appear to be reasonable.

Monte Carlo Analysis

- Parameters are varied randomly and output statistics are gathered.
- We use programs like MATLAB, Mathcad, or a spreadsheet to complete a statistically significant set of calculations.
- For example, with Excel®, a resistor with 5% tolerance can be expressed as:

$$R = R_{nom} (1 + 2\varepsilon(\text{RAND}() - 0.5))$$

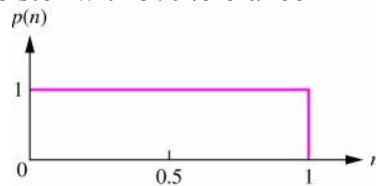The RAND() function returns random numbers uniformly distributed between 0 and 1.




Monte Carlo Analysis Example

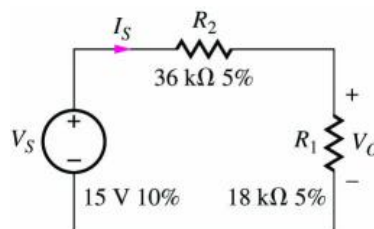Problem: Perform a Monte Carlo analysis and find the mean, standard deviation, min, and max for V_o , I_s , and power delivered from the source.

Solution:

- **Known Information and Given Data:** Circuit topology and values in figure.
- **Unknowns:** The mean, standard deviation, min, and max for V_o , I_s , and P_s .
- **Approach:** Use a spreadsheet to evaluate the circuit equations with random parameters.
- **Assumptions:** None.
- **Analysis:** Next slides...



Monte Carlo parameter definitions:

$$V_s = 15(1 + 0.2(\text{RAND}() - 0.5))$$

$$R_1 = 18,000(1 + 0.1(\text{RAND}() - 0.5))$$

$$R_2 = 36,000(1 + 0.1(\text{RAND}() - 0.5))$$

Monte Carlo Analysis Example (cont.)

Nominal Source current:

$$I_S^{nom} = \frac{V_S^{nom}}{R_1^{nom} + R_2^{nom}} = \frac{15V}{18k\Omega + 36k\Omega} = 278\mu A$$


Rewrite V_o to help us determine how to find the worst-case values.

$$V_o = V_S \frac{R_1}{R_1 + R_2} = \frac{V_S}{1 + \frac{R_2}{R_1}}$$

V_o is maximized for max V_S , R_1 and min R_2 .
 V_o is minimized for min V_S , R_1 , and max R_2 .

$$V_o^{max} = \frac{15V(1.1)}{1 + \frac{36K(0.95)}{18K(1.05)}} = 5.87V \quad V_o^{min} = \frac{15V(0.95)}{1 + \frac{36K(1.05)}{18K(0.95)}} = 4.20V$$

Monte Carlo Analysis Example (cont.)

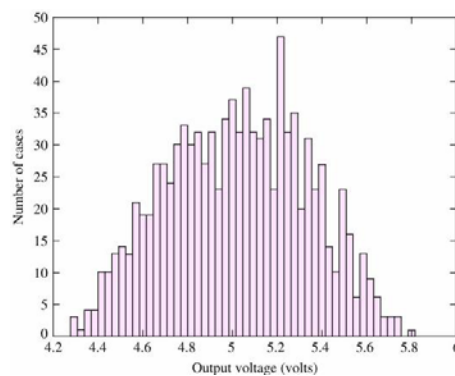

Histogram of output voltage from 1000 case Monte Carlo simulation.

See table 5.1 for complete results.



Temperature Coefficients

- Most circuit parameters are temperature sensitive.

$$P = P_{\text{nom}}(1 + \alpha_1 \Delta T + \alpha_2 \Delta T^2) \text{ where } \Delta T = T - T_{\text{nom}}$$

P_{nom} is defined at T_{nom}

- Most versions of SPICE allow for the specification of T_{NOM} , T , $TC1(\alpha_1)$, $TC2(\alpha_2)$.
- SPICE temperature model for resistor:
 $R(T) = R(T_{\text{NOM}}) * [1 + TC1 * (T - T_{\text{NOM}}) + TC2 * (T - T_{\text{NOM}})^2]$
- Many other components have similar models.