 


University of Padova,
Dept. of Information Engineering

2015 Summer School of Information Engineering

ICT for Automotive Industry



Bressanone (BZ), Italy
July 5 - 11, 2013



Automotive Smart Power IC Design, 2015 Summer School of Information Engineering, University of Padova, Italy
© 2015 Bernhard Wicht, Robert Bosch Center for Power Electronics, Reutlingen University, Germany

1

University of Padova
Dept. of Information Engineering

2015 Summer School of Information Engineering

ICT for Automotive Industry

Automotive Smart Power IC Design

Bressanone / Brixen (BZ), Italy, July 8, 2015



Prof. Dr.-Ing. Bernhard Wicht
Robert Bosch Center for Power Electronics
Reutlingen University, Germany



Robert Bosch Zentrum für Leistungselektronik
Hochschule Reutlingen • Universität Stuttgart • Robert Bosch GmbH



Hochschule Reutlingen
Reutlingen University



Automotive Smart Power IC Design, 2015 Summer School of Information Engineering, University of Padova, Italy
© 2015 Bernhard Wicht, Robert Bosch Center for Power Electronics, Reutlingen University, Germany

2

Contact: Prof. Dr.-Ing. Bernhard Wicht
Robert Bosch Center for Power Electronics
Reutlingen University
Alteburgstr. 150
72762 Reutlingen, Germany
Phone: +49-7121-2717090
bernhard.wicht@reutlingen-university.de
www.rbzentrum.de




Outline

1. Overview and Introduction
2. Power Switches
3. Gate Drivers
4. Protection, Monitoring and Sensing
5. Charge Pumps
6. Voltage Regulators
7. System Design

1. Overview and Introduction
 2. Power Switches
 3. Gate Drivers
 4. Protection, Monitoring and Sensing
 5. Charge Pumps
 6. Voltage Regulators
 7. System Design

rbz Automotive Smart Power IC Design, 2015 Summer School of Information Engineering, University of Padova, Italy
 © 2015 Bernhard Wicht, Robert Bosch Center for Power Electronics, Reutlingen University, Germany

5

 


Example: Electronic Stability Program (ESP)





Power Control Unit contains integrated power FETs for 12 solenoids → 1-2A per solenoid (connected to car battery)

 Example: Electronic Stability Program (ESP)



Smart Power

  Smart Power = Integration of analog, digital und power on one single IC → Advantage: higher integration



One IC to replace multiple modules, additional monitoring and diagnosis functions → cost reduction, increased reliability, innovation through new functionality

Smart Power

Smart Part	Power Part
Over temperature Short circuit Open load Over voltage Under voltage Current limiting Load dump protection Control Loops (e.g. PWM)	High-voltage nmos / pmos High-side switch  Low-side switch 
Digital CMOS 1.8V, 3V MOS + bipolar Analog 1.8V, 3V, 5V	DMOS, Drain-extended MOS 5V, 12V,..., 80V and ~1A

Other technology features

- Buried layer or trench isolation
- Zener diodes, schottky and power diodes
- OTP memory, EEPROM, Flash memory

Mixed Signal Systems in Automotive

Power Train / Engine Control

- Sensor Signal Conditioning
- Transmission Control
- Fuel Injection Drivers
- Power Management



Dashboard

- LED Drivers
- Power Management



Body

- Window Lifter / Mirror Drivers
- Door Lock Solenoid Drivers
- Passive/Keyless Entry
- Relay Drivers
- Exterior Lightning (LED Drivers)

Safety Systems

- Airbag
- Passenger Recognition
- Adaptive Cruise Control
- Collision Avoidance



Chassis Systems

- ABS Controllers
- Vehicle Stability (ESP)
- Electronic Power Steering
- Collision Avoidance

Infotainment

- Performance Audio
- Navigation
- Power Management

Energy Management


- Hybrid Vehicle
- Advanced Alternator System
- Motor Management

Vehicle Networking

- LIN
- CAN
- Flexray
- System Base Chips



Example: Engine Management

 


Engine Management ASIC

Source: Bosch




Electric Vehicle System

 

Source: Bosch

Smart Power – Future Markets

 Smart Power ICs are enabler for growth areas like smart home and voltage conversion from renewable energy



Source: Bosch

Automotive Trends and Drivers

Example: Driver Assistance

Park assist, blind spot detection, lane departure warning, night vision, adaptive cruise control, traffic sign recognition, object recognition



Example: Infotainment

Central entertainment unit, navigation, car audio, emergency call, WiFi, wireless USB, flash card slot, USB port, bluetooth


Example: Hybrid / Electrical vehicles

Start/Stop, battery monitoring, cell balancing, supercap management, DC/DC systems, inverter systems, charging solutions (including charging stations), fuel cells



 Example: Vehicle Safety


Emerging countries starting legislative agendas on vehicle safety → ABS, ESP



The Electrical Network in a Car

Voltage systems:

 - Cars: 12V standard (battery peak power: 10kW!)
- Truck: 24V (=2x 12V in series)
- New solutions for hybrid or electrical cars: 12V, 48V + HV




The battery line noise is modeled by ISO test pulses (also known as Schaffner pulses), defined by ISO 7637-2

Automotive IC Operating Conditions

Typical Device Ratings

	Minimum	Maximum
Supply voltage	4 - 6V	16 - 25V
Transient on supply	36V	60V
Reverse battery protection		-14V
Quiescent current		1 - 5 μ A
ESD strike (HBM)		2 - 6kV
Ambient temperature	-40°C	125°C
Junction temperature	-40°C	>150°C

 


1. Overview and Introduction
2. **Power Switches**
3. Gate Drivers
4. Protection, Monitoring and Sensing
5. Charge Pumps
6. Voltage Regulators
7. System Design


 Automotive Smart Power IC Design, 2015 Summer School of Information Engineering, University of Padova, Italy
© 2015 Bernhard Wicht, Robert Bosch Center for Power Electronics, Reutlingen University, Germany

Power Transistor Switches & Drivers


Low-Side

 


High-Side

 

Half-Bridge

 

Full or H-Bridge

 

- Transistors can be on-chip (integrated) or discrete (external)
- Most applications use n-type transistors due to lower on-resistance R_{DSon}

Applications:

- Motor Control
- Valves / Solenoids
- Switched Mode Supplies
- Relais, Warning Lamps, LEDs




Automotive Smart Power IC Design, 2015 Summer School of Information Engineering, University of Padova, Italy
© 2015 Bernhard Wicht, Robert Bosch Center for Power Electronics, Reutlingen University, Germany

19


Power Transistors

Discrete Power FET
(external component)

 

On-resistance $\sim 10 \dots 100 \text{m}\Omega$
Drain Currents $> 1 \dots 10 \text{A}$

 Integrated power FET in
High-Voltage BiCMOS
Technologies



On-resistance $< 1 \Omega$
Drain Currents $< 1 \dots 2 \text{A}$
FET types for $> 60 \text{V}$ available




Automotive Smart Power IC Design, 2015 Summer School of Information Engineering, University of Padova, Italy
© 2015 Bernhard Wicht, Robert Bosch Center for Power Electronics, Reutlingen University, Germany


20

Power MOSFET = DMOS

 DMOS = Double Diffused MOS (lateral oder vertical)



 - Low on-resistance R_{DSon} ($< 1\Omega$, 1-2A), large V_{DSmax}
- Source and Gate isolated from Substrat \rightarrow negative voltages possible
- Parasitic Diodes D-S and D-SUB \rightarrow have to be taken care of \rightarrow can be utilized as free-wheeling or power diode



Power Transistor Sizing

- Design W/L for targeted R_{DSon} (over all corners!)
- Switch = Triode-Region $\rightarrow W/L$ and V_{GS} determine R_{DSon}
- Trade-off between area and R_{DSon}
e.g. $R_{DSon} = 0.5\Omega \rightarrow W/L = 200 \cdot (450\mu\text{m}/1.8\mu\text{m}) \rightarrow (0.5 \times 1.5)\text{mm}^2$
- W and L define gate capacitance \rightarrow to be (dis-)charged during switching $\rightarrow C_{gate} \sim 0.1...1\text{nF}$





Power Transistors: Dropout

Dropout V_{do} (i.e. R_{DSon}) determines W/L and drives decision for pmos or nmos



Smaller dropout extends battery lifetime

Example: Linear voltage regulator

  

Transistor Switching Behavior and Losses

For inductive loads:

  

Example:

$$V_{GS} = 8V$$

$$V_{th} = 2V$$

$$I_D = 0.5A$$

$$R_{DSon} = 0.5\Omega$$

$$V_{DS} = 12V$$

$$t_{sw} = 100ns$$

$$f_s = 500kHz$$

Transition Losses:


$$0,5 V_{DS} I_D f_s t_{sw} = 150mW$$

Conduction Losses:

$$I_D^2 R_{DSon} = 250mW$$


Parasitic Effects

 For $V_D < 0$ substrate currents through parasitic npn:



Consequence:
 - Disturbance of other circuit blocks
 - Debiasing, latch-up

 Countermeasure: Guardrings (GR) around the LDMOS




GR around every drain which goes to an IC Pin
 Drawback: Layout area \rightarrow cost!

Isolation of Circuit Blocks


Every circuit block can be placed in isolation
 \rightarrow Shielding against substrate noise coupling
 \rightarrow similar to guardring with full "incapsulation" (also at bottom)

 Rule for smart power designs: Isolate every circuit block if possible



Substrate Coupling

 Voltage slopes > 10V/ns cause capacitive charging currents in the order of 100mA on IC-level during transition





- Substrate debiasing >4V
- Malfunction of analog and digital circuits

Substrate Coupling: Experimental Results


MHz-Converter

Test chips with / without BSM

Test chip layout

  

Measured disturbance at 40V/ns:

 

- Back-Side Metallization (BMS) reduces coupling by ~100%
- p-Guardring is less efficient but readily available

1. Overview and Introduction
2. Power Switches
3. Gate Drivers
4. Protection, Monitoring and Sensing
5. Charge Pumps
6. Voltage Regulators
7. System Design

rbz Automotive Smart Power IC Design, 2015 Summer School of Information Engineering, University of Padova, Italy
© 2015 Bernhard Wicht, Robert Bosch Center for Power Electronics, Reutlingen University, Germany

29

Gate Driver Block Diagram and Circuits

Main circuit blocks:

- Power FET (n/p-type)
- Protection
- LS / HS Driver
- Levelshifter
- Gate supply
- Dead Time Control (only for bridges)


rbz Automotive Smart Power IC Design, 2015 Summer School of Information Engineering, University of Padova, Italy
© 2015 Bernhard Wicht, Robert Bosch Center for Power Electronics, Reutlingen University, Germany

30

Low-Side Driver

Function: Turn-on/off power switch with sufficient gate overdrive (voltage) and appropriate driving capability (current over time)

Principle:

 


Parameters:

- Gate driver sink / source resistance (at given I_{gate})
- Sink / source peak current


Low-Side Driver

Circuit structure:


 


- Levelshifter followed by driver stage(s) (“CMOS inverter”)
- Single driver stage if small power FET (low C_{gate})
- Cascaded driver stages if large power FET (large C_{gate})

Practical Implementation of Gate Drivers

 

  Reference: S. Hitzler, B. Wichterle et al., ESSCIRC 2009



$W/L = 32000\mu\text{m} / 2.5\mu\text{m}$
 15ns delay at $C_{gate} = 10\text{nF}$

Driver resistance: 3Ω
 Driver peak current: 1.5A



Optimization for speed, power, area: n stages, each increasing in driver strength (W/L) by Faktor α



High-Side Driver

Type 1 Floating Driver

Type 2 Referred to GND

  


General:

- Overdrive needed $\rightarrow V_{high} = V_{bat} + V_{GS}$
- V_{high} from charge pump, boost converter, bootstrapping



High-Side Driver



Example for floating driver (Type 1)

 

- Driver stage: Low voltage transistors even for 60V V_{BAT}
- R_{pu} : Tradeoff between speed and DC current (typ. 100k Ω)
- Diode(s) to clamp voltage across R_{pu} and limit V_{GS} for driver

High-Side Gate Supply: Bootstrapping

  Similar to charge pump with oscillator replaced by bridge



- C_{boot} supplies high-side driver $\rightarrow V_{boot} = V_{BAT} + V_{DD} - V_F$
- C_{boot} gets recharged if high-side is off (low-side on, $V_{phase} = 0V$) from V_{DD} through bootstrapping diode D_{boot}
- Sizing: $C_{boot} \geq (Q_{gate} + Q_{rr} + I_{boot}/f_{sw}) / \Delta V_{boot}$


Levelshifters

Resistor-based Levelshifter




- DC current
- + Simple, small
- + Default state

Cross-coupled Levelshifter

 

- + No DC current from V_{HIGH}
- Slow and large area
- No default state



High-voltage version with cascodes

 

Advanced levelshifters combine advantages of both (often with capacitive coupling), bus protocol to save # of levelshifters


Cross-coupled Levelshifter with Full HS Swing

  V_{SG} of cascodes M5, M6 prevents logic '0' level at driver input
→ full high-side swing achieved by active clamping → M7, M8




Insertion of inverters in cross-coupling (right) → increased loop gain → faster switching and reduced power consumption
→ M7, M8 can become minimum size

50V High-Speed dv/dt Robust Levelshifter

 

 
- Minimum pulse width <math>< 3\text{ ns}</math>
- 5 ns propagation delay
- Robust against transitions >20 V/ns:
No incorrect switching at >2 mA coupling currents



Reference: J. Wittmann, Th. Raehl, B. Wicht, "A 50V High-Speed Level Shifter with High dv/dt Immunity for Multi-MHz DDC Converters", ESSIRIC 2014

Dead Time Control of HS / LS Drivers

 To avoid cross-conduction of HS and LS FET (damage!):
Turn off FET → then turn on FET with dead time in between




Methods:

- Constant delay: Simple, but worst case margin → large t_{dead}
- Adaptive delay: Sensing of off-state → then turn on other FET
- Predictive delay: Cycle-by-cycle control by sensing LS body diode or switching node → good performance, but complex

Synchronous Buck with Dead Time Control

 $V_{in} = 12-18V$, 10 MHz buck converter with predictive mixed-signal dead time control based on a 125 ps 8-bit differential delay chain




Reference: J. Wittmann, A. Barner, Th. Rosahl, B. Wicht, "A 12V 40MHz Buck Converter with Dead Time Control Based on a 125 ps Differential Delay Chain", ESSCIRC, 2015

- No low-side body diode conduction
- Loss reduction of up to 30% → 6% higher efficiency at 10 MHz

 1. Overview and Introduction
2. Power Switches
3. Gate Drivers
4. Protection, Monitoring and Sensing
5. Charge Pumps
6. Voltage Regulators
7. System Design


Protection and Diagnostics in Smart Power

- Thermal protection
- Over-voltage (VDS)
- Over-current
- Short-to-ground
- Short-to-battery
- Open load
- Under-voltage (UVLO)



Thermal Shutdown

 
Protects the IC from damage at high temperature




Usually installed as a secondary protection:
Indirect limitation of load current in regulators, drivers

Protection Schemes - Inductive Loads

 
Low-side and high-side switches: Zener diode based voltage clamps ensure $V_{DS} < V_{DSmax}$ when power switch is turned off



 Over-Current Protection – Current Sensing



Safe Operating Area (SOA)

 

Open loop:

- Over-current detection → turn-off power FET
- Continuous current measurement


Closed loop:

- Current limit (example: LDO)
- Current controlled DCDC conversion


Current Sensing



- + Lossless
- Accuracy

 

 - + Lossless
- + Good accuracy
- Complexity



Accuracy depends on (1) mismatch in sense transistor ratio M , (2) amplifier offset and on variation of (3) R_{out} (use trimming), (4) total loop gain


References:
 • W.H. Ki, Current sensing technique..., U.S. Patent 5,757,174, May 26, 1998.
 • D. Ma et al., A 1.8V single-inductor dual-output..., IEEE VLSI Symp. Circ., June 2001
 • H. Y. H. Lam et al., Loop gain analysis and ..., ISCAS 2004.



Monitoring: Short to GND / BAT, Open Load


Short to battery usually detected by current limit

 Short to ground, open load are detected in off-state (FET off):



 Voltage levels: $V_{ref2} < V_{DD} - V_F - I_{diag} \cdot R_{diag} < V_{ref1}$






1. Overview and Introduction
2. Power Switches
3. Gate Drivers
4. Protection, Monitoring and Sensing
- 5. Charge Pumps**
6. Voltage Regulators
7. System Design

rbz Automotive Smart Power IC Design, 2015 Summer School of Information Engineering, University of Padova, Italy
 © 2015 Bernhard Wicht, Robert Bosch Center for Power Electronics, Reutlingen University, Germany


49

Charge Pump Principle

Idea (Dickson Charge Pump):

 


With buffer C at output:

 


Voltage doubler: $V_{out} = 2V_{in}$ (ideally with $I_{load} = 0$)

Transient and DC Behavior

Without load current:

 


 With load \rightarrow ripple and drop of V_{out}




With I_{load} , C_{par} and finite switch on-resistance R_{on}
 
$$V_{out} = V_{in} + V_{in} \frac{C_p}{C_p + C_{par}} - \frac{I_{load}}{f_{sw}(C_p + C_{par})} - 2R_{on}I_{load}$$




Typical Charge Pump Implementations

With diodes:

 

$$V_{out} |_{t \rightarrow \infty} = 2(V_{DD} - V_F)$$

With transistors:

 

$$V_{out} |_{t \rightarrow \infty} = 2(V_{DD} - V_{DS,on})$$


Reference: Pelliconi, ESSCIRC 2001 und JSSC 2003

Advantage: Dual phase operation
 \rightarrow 2x driving capability
 \rightarrow 50% ripple or reduction of C , f

Cascading of N stages possible: $V_{out} = (N+1) V_{in}$


Realization of Diodes

 Every diode is associated with parasitic bipolar transistor:



Charge Pump Power Efficiency

Equivalent circuit with major losses:

 


Charge pump efficiency

$$\eta = \frac{P_{out}}{P_{in}} = \frac{V_{out} I_{out}}{V_{in} I_{in}} = \frac{\overline{V_{out}} \overline{I_{out}}}{V_{in} \overline{I_{in}}} \left. \vphantom{\frac{P_{out}}{P_{in}}} \right\} \text{Mean values per periode to account for ripple, current peaks, etc.}$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{(2V_{in} - V_{loss1} - V_{loss2} - \dots) I_{out}}{V_{in} (2I_{out} + I_{loss1} + I_{loss2} + I_{loss3} + \dots)}$$

EMC: Conducted Emissions

 



Reference: Wittmann, Wicht, "Charge Pump Design for Low EMC - Implementation, Simulation and Measurements", ISCAS 2011

Current spikes from switching circuits like oscillator, charge pump \rightarrow noise on global connection lines

Current-mode Charge Pumps

Switches replaced by current sources at bottom of C_p \rightarrow reduced current spikes \rightarrow EMC advantage

Conventional hard switching charge pump:

  


Periodic current spikes at every recharge of C_p

„Slow“ recharge of C_p over one half periode

Automotive Power Management


Multiple regulators to supply μ Cs, MPUs, DSPs, analog & mixed-signal circuits \rightarrow at „point of load“

 \rightarrow Part of smart power ICs or separate power management ICs



Automotive:

 $V_{in} > 10 - 60V$,
larger conversion ratios




In Comparison \rightarrow Handheld devices, consumer products:

$V_{in} \sim 4V$, moderate conversion ratios

How to Convert 12V into 2V?

Using a simple resistor...

It works, but...

 

Large power loss at the resistor:



$$P_R = V_R \cdot I = 10V \cdot 1A = 10W$$

(even larger than P_{out} !)

Linear Low Dropout Regulator (LDO)

Key characteristics:

  - + Fast load transient response (load steps)
- Poor power efficiency (losses in power FET)



Reference: Willmann, Wicht ISCAS 2011

Area comparison:
„nmos + CP < pmos“


→ Dropout drives decision for pmos or nmos




Reverse Polarity Protection

Rule: n-well at highest potential

 
→ pn-junction to substrate reverse biased




Concept:

 

Option 1:

 

Option 2:

 


Most simple solution: Diode in battery line

→ drawback: dropout reduced by V_F → often not acceptable



Shunt Regulator

 
Alternative to LDO, often as a crude supply for e.g. noncritical digital block or as pre-regulator for LDO



Comparison to LDO: Open loop → fast, but not as precise

How to Convert 12V into 2V?

 
Switched mode conversion... It works and has small losses...



Power loss at the switches: $P_S = V_S \cdot I_S$

ideally:
off: $I_S = 0 \rightarrow P_S = 0$
on: $V_S = 0 \rightarrow P_S = 0$


Pulse-Width Modulation:

 

in reality >95% power efficiency possible

Switched Mode Power Supplies

 
Key advantage: Much higher efficiency (>95%) and much less heat than linear regulators because L stores the energy



Impact of Fast Switching and High Vin

Buck converter:
 
$$t_{on} = \frac{V_{out}}{V_{in}} \cdot \frac{1}{f_{sw}}$$




Losses

Power loss scales with switching frequency: $P_{loss} = E_{loss} f_{sw}$


Capacitive energy loss scales proportional to V_{in}^2

Switching energy loss scales proportional to V_{in} :
 
$$E_{sw} = I_{out} V_{in} \Delta t_{sw} = 1A \cdot 50V \cdot 1ns = 50nJ \text{ (per period)}$$



Challenges for Fast Switching Converters


 


Regulation Schemes: Voltage Mode Control

Control voltage V_c is compared to sawtooth reference:

$$D = t_{on} / T = V_c / V_{smax} \rightarrow D \uparrow \text{ if } V_c \uparrow$$

  
Voltage mode control (direct duty control)



Drawback:

- Poor transient response to changes of $V_{in} \rightarrow$ Change in D has $L-C_{out}$ time constant
- Acceptable line regulation requires voltage feedforward

Control Loop Analysis and Stability

 



Closed loop transfer function: $\frac{V_{out}}{V_{ref}} = \frac{1}{\alpha} \frac{G(s)H(s)}{1 + G(s)H(s)} \approx \frac{1}{\alpha}$ $\alpha = \frac{R_2}{R_1 + R_2}$

Loop gain: $\frac{V_{fb}}{V_{ref}} = G(s)H(s)$

Modulator transfer function: $G(s) = \frac{1}{V_{smax}} V_{in} \frac{1}{1 + s \frac{L}{R} + s^2 LC_{out}}$


Regulation Schemes: Current Mode Control

  V_c is compared to a ramp voltage V_{sense} derived from the inductor current I_L , forming a second, inner control loop



- Excellent line transient response $\rightarrow V_{out}$ independent of V_{in}
- Inherent I_L current limit (by limiting V_c)

 Control Loop Analysis Current Mode Control




Current Mode: Subharmonic Oscillations

Unconditional instability above 50% duty cycle \rightarrow perturbation ΔI_L of inductor current leads to subharmonic oscillations

$D < 0.5$
(stable)

$D > 0.5$
(unstable)

$D > 0.5$
(with slope compensation)

 


\rightarrow stable if

$$m > \frac{m_2}{2}$$

Regulation Schemes: Current Mode Control

 With slope compensation: $(V_c - V_{slope})$ is compared to a ramp voltage V_{sense} derived from the inductor current




Two options to implement slope compensation

Slope Compensation: Example for Option 2


Difference ($V_c - V_{slope}$) is generated in current domain, fed into replica FET and compared to voltage across power
 
$$FET = V_{sense} = V_{phase} = R_{DSon} \cdot I_L$$



Concept can also be implemented on high-side FET

 State-of-the-Art: Efficiency vs. fsw and Vin



- Existing high Vin converters are operating at < 5MHz
- Technology / circuits set limit at ~30 MHz (conversion ratio)
- Gap within 5-30 MHz not covered yet

1. Overview and Introduction
2. Power Switches
3. Gate Drivers
4. Protection, Monitoring and Sensing
5. Charge Pumps
6. Voltage Regulators
7. System Design

 Automotive Smart Power IC Design, 2015 Summer School of Information Engineering, University of Padova, Italy
 © 2015 Bernhard Wicht, Robert Bosch Center for Power Electronics, Reutlingen University, Germany

77

Floorplan

Rule: Separate high-voltage and low-voltage domains
 Motivation: HV-Isolation = Spacing = Chip Area = Cost

Source: ATMEL, Automotive Compilation, 2010


Mechanical stress: avoid corners / edges for critical blocks

 Automotive Smart Power IC Design, 2015 Summer School of Information Engineering, University of Padova, Italy
 © 2015 Bernhard Wicht, Robert Bosch Center for Power Electronics, Reutlingen University, Germany


78

Pinout, Grounding and Supply Guidelines

- Supply and ground pin next to each other, bypass-C placed here close to pins → reduces inductive effect and reduces EMI radiation level, also valid for on-chip wiring
- Keep short bond wires for power pins and fast signals ($R \downarrow$, $L \downarrow$) → close to the middle of one side of the die, vice versa: corner pins for quite signals
- Use separate bond pads for each domain or at least apply star connections, consider double / tripple-bond
- IC-Level wiring in groups:
 - Supply lines (high current)
 - Sensitive lines (analog)
 - Noisy lines (digital, switching power)

 


Pinout, Grounding and Supply Guidelines

 

Packaging, Metallization and Thermal Design


Selecting the proper package

 - Die Size estimation
- Power Dissipation




IC Level Copper Technology

 - Power bussing
- Reduces power device area
- Bond Over Active Circuitry



Thermal Analysis

 - Simple hand calculations
- Detailed thermal simulations



Source: Texas Instruments



Thanks for Your Attention!

Reutlingen and Surroundings

